

DIGITAL SYSTEM LABORATORY WORK
FLIP-FLOP APPLICATION



BY :
NADHIFAH CHAIRUNNISA
L200184137

INFORMATION TECHNOLOGY
FACULTY OF COMUNICATION AND INFORMATICS
UNIVERSITY OF MUHAMMADIYAH SURAKARTA


Name : Nadhifah Chairunnisa

NIM : L2001841137

Assistent Name : Salsa Sasmita Mukti

Date of Practicum : may 17, 2019

Attempt 1 : Make counter JK-FF

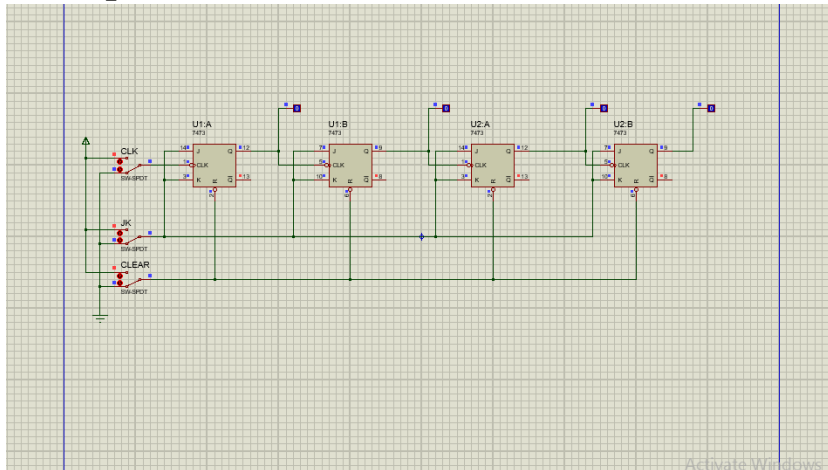

1.

2. Simulation the circuit

	INPUT			OUTPUT			
	CLEAR	JK	CLK	A	B	C	D
1.	1	1	0	0	0	0	0
2.	1	1	1	0	0	0	0
3.	1	1	0	0	0	0	1
4.	1	1	1	0	0	0	1
5.	1	1	0	0	0	1	0
6.	1	1	1	0	0	1	0
7.	1	1	0	0	0	1	1
8.	1	1	1	0	0	1	1
9.	1	1	0	0	1	0	0
10.	1	1	1	0	1	0	0
11.	1	1	0	0	1	0	1
12.	1	1	1	0	1	0	1
13.	1	1	0	0	1	1	0
14.	1	1	1	0	1	1	0
15.	1	0	0	0	1	1	0
16.	1	0	1	0	1	1	0
17.	1	1	0	0	1	1	1

18.	1	1	1	0	1	1	1
19.	0	1	0	0	0	0	0
20.	0	1	1	0	0	0	0


3. The Function

- Switch of CLK : Binary Saver
- Switch of JK : As a First counter
- Switch of CLEAR : To rearrange the condition of switch of JK

4. Inference

Output will be change if switch of CLK = 0, and output will be same if switch of JK = 0, and output not run or 0 if switch of CLEAR = 0

Attempt 2 : Counter MOD 10

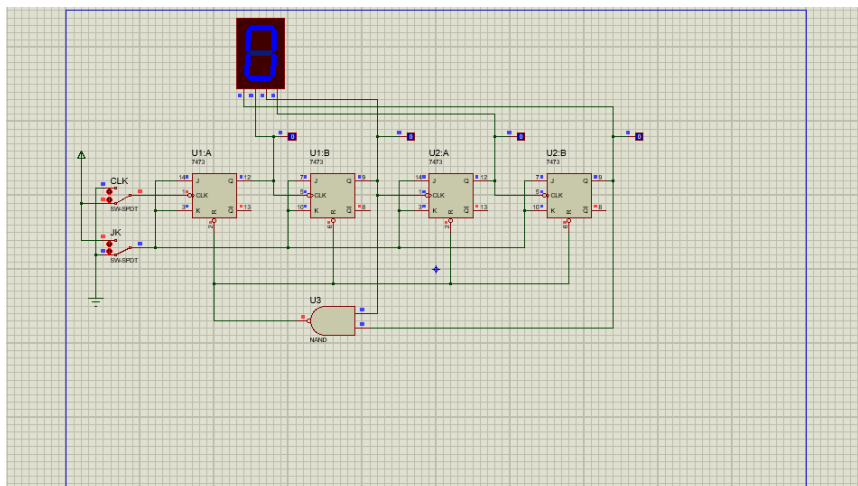

1.

2. Simulation the Circuit

	INPUT		OUTPUT			
	JK	CLK	A	B	C	D
1.	1	0	0	0	0	0
2.	1	1	0	0	0	1
3.	1	0	0	0	0	1
4.	1	1	0	0	1	0
5.	1	0	0	0	1	0
6.	1	1	0	0	1	1
7.	1	0	0	0	1	1


8.	1	1	0	1	0	0
9.	1	0	0	1	0	0
10.	1	1	0	1	0	1
11.	1	0	0	1	0	1
12.	1	1	0	1	1	0
13.	1	0	0	1	1	0
14.	1	1	0	1	1	1
15.	1	0	0	1	1	1
16.	1	1	1	0	0	0
17.	1	0	1	0	0	0
18.	1	1	1	0	0	1
19.	1	0	1	0	0	1
20.	1	1	0	0	0	0
21.	0	0	0	0	0	0
22.	0	1	0	0	0	0
23.	1	0	0	0	0	0
24.	1	1	0	0	0	1

3. Inference

Output will be change if switch of JK and CLK is on or = 1

Attempt 3 : Make Register JK-FF

1.

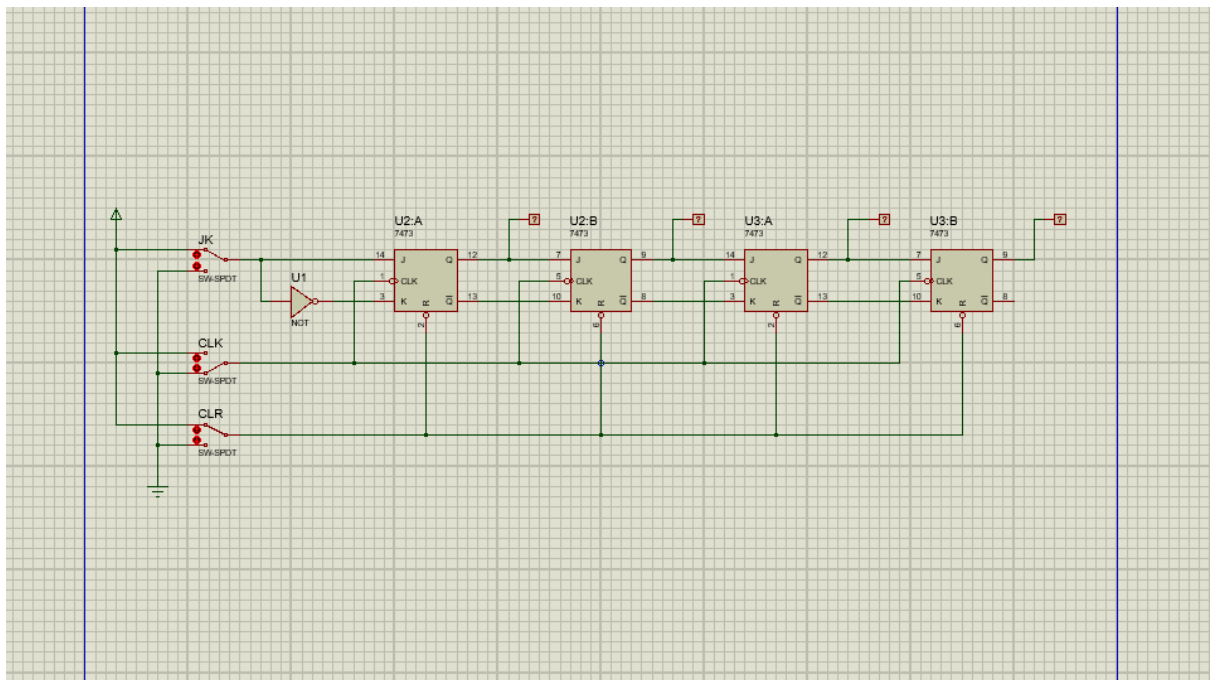

2. Simulation the switch

	CLR	JK	CLK	A	B	C	D
1.	0	X	-	0	0	0	0
2.	1	1	-	0	0	0	0
3.	1	1	<i>1</i>	0	0	0	1
4.	1	1	2	0	0	1	1
5.	1	1	3	0	1	1	1
6.	1	0	4	1	1	1	0
7.	1	0	5	1	1	0	0
8.	1	0	6	1	0	0	0
9.	1	0	7	0	0	0	0
10.	1	0	8	0	0	0	0
11.	1	1	9	0	0	0	1
12.	1	0	<i>10</i>	0	0	1	0
13.	1	0	<i>11</i>	0	1	0	0
14.	1	0	<i>12</i>	1	0	0	0
15.	1	0	<i>13</i>	0	0	0	0

3. Inference

if switch of CLEAR is off or 0, output cant be change. If switch of JK is on so output start from D and if off output start from A. And output can be change if switch of CLOCK is 0 or off